

BCD Counter with T Flip-Flops

Abhimanyu Koushik EE24BTECH11024

April 6, 2025

Abstract

This document details the design and implementation of a bidirectional BCD counter using T flip-flops. The counter, which counts from 0 to 9 (and vice versa), employs additional logic to skip invalid BCD states. The design includes detailed state tables, Karnaugh maps, and circuit diagrams.

Aim

To design and implement a BCD (Binary Coded Decimal) counter using T flip-flops that can count both up and down based on input conditions, with a maximum count of 9 (0–9).

Apparatus

- JK Flip-Flops (IC 7476) configured as T flip-flops (by tying J and K high) – 4 units
- Logic gates (AND, OR, XOR, NOT gates)
- Push buttons (2 units – one for up counting, one for down counting)
- 7-segment display with BCD to 7-segment decoder
- Power supply (5V DC)
- Breadboard and jumper wires
- Resistors (1k Ω , 330 Ω)
- Arduino board (for clock generation and power)
- Oscilloscope (to verify clock signals)
- Logic analyzer (to verify state transitions)

Theory

A BCD counter is a digital counter that counts from 0 (0000) to 9 (1001) in binary and then resets back to 0. In this experiment, we implement a bidirectional BCD counter using T flip-flops that can count both up and down based on input signals.

T Flip-Flop

T flip-flops (Toggle flip-flops) change their output state when triggered by a clock pulse if their T input is 1. If $T = 0$, the output remains unchanged. This makes them ideal for counter applications.

The characteristic equation of a T flip-flop is:

$$Q^+ = Q \oplus T$$

where:

- Q^+ is the next state,
- Q is the current state,
- T is the toggle input,
- \oplus represents the XOR operation.

A T flip-flop can be constructed from a JK flip-flop by connecting both J and K inputs to the same signal T . When $T = 1$, the flip-flop toggles on each clock pulse; when $T = 0$, it maintains its state.

BCD Counter

A BCD counter counts from 0 to 9 in binary (0000 to 1001) and then resets to 0. Since a 4-bit binary counter can represent 16 states (0–15), additional logic is required to skip the invalid states (10–15). This counter is known as a modulo-10 counter.

Up/Down Counter Operation

An up/down (bidirectional) counter can count in both ascending and descending sequences based on a control input. The mode signal M controls the direction:

- $M = 0$: Up counting mode (0 to 9, then resets to 0)
- $M = 1$: Down counting mode (9 to 0, then resets to 9)

7-Segment Display

The 7-segment display consists of seven LEDs arranged in a pattern to display decimal digits. A BCD-to-7-segment decoder converts the 4-bit BCD output from the counter into signals that illuminate the appropriate segments (labeled 'a' through 'g') to display digits 0–9.

Derivation of Logic

Below are the state tables and Karnaugh map derivations for both the up and down counter modes.

State Tables

Up Counter State Table:

Present State				T Flip-Flops				Next State			
Q_3	Q_2	Q_1	Q_0	T_3	T_2	T_1	T_0	Q_3	Q_2	Q_1	Q_0
0	0	0	0	0	0	0	1	0	0	0	1
0	0	0	1	0	0	1	1	0	0	1	0
0	0	1	0	0	0	0	1	0	0	1	1
0	0	1	1	0	1	1	1	0	1	0	0
0	1	0	0	0	0	0	1	0	1	0	1
0	1	0	1	0	0	1	1	0	1	1	0
0	1	1	0	0	0	0	1	0	1	1	1
0	1	1	1	1	1	1	1	1	0	0	0
1	0	0	0	0	0	0	1	1	0	0	1
1	0	0	1	1	0	0	1	0	0	0	0
1	0	1	0	X	X	X	X	X	X	X	X
1	0	1	1	X	X	X	X	X	X	X	X
1	1	0	0	X	X	X	X	X	X	X	X
1	1	0	1	X	X	X	X	X	X	X	X
1	1	1	0	X	X	X	X	X	X	X	X
1	1	1	1	X	X	X	X	X	X	X	X

Table 1: State table for the single-digit BCD Up-counter. (X denotes don't-care conditions.)

Down Counter State Table:

Present State				T Flip-Flops				Next State			
Q_3	Q_2	Q_1	Q_0	T_3	T_2	T_1	T_0	Q_3	Q_2	Q_1	Q_0
0	0	0	0	1	0	0	1	1	0	0	1
0	0	0	1	0	0	0	1	0	0	0	0
0	0	1	0	0	0	1	1	0	0	0	1
0	0	1	1	0	0	0	1	0	0	1	0
0	1	0	0	0	1	1	1	0	0	1	1
0	1	0	1	0	0	0	1	0	1	0	0
0	1	1	0	0	0	1	1	0	1	0	1
0	1	1	1	0	0	0	1	0	1	1	0
1	0	0	0	1	1	1	1	0	1	1	1
1	0	0	1	0	0	0	1	1	0	0	0
1	0	1	0	X	X	X	X	X	X	X	X
1	0	1	1	X	X	X	X	X	X	X	X
1	1	0	0	X	X	X	X	X	X	X	X
1	1	0	1	X	X	X	X	X	X	X	X
1	1	1	0	X	X	X	X	X	X	X	X
1	1	1	1	X	X	X	X	X	X	X	X

Table 2: State table for the single-digit BCD Down-counter. (X denotes don't-care conditions.)

Karnaugh Maps for T Flip-Flops

Up Counter T Flip-Flops

For T_0 :

Since $T_0 = 1$ for all cases, no Karnaugh map is required.

For T_1 :

		Q_1Q_0			
		00	01	11	10
Q_3Q_2	00	0	1	1	0
	01	0	1	1	0
	11	X	X	X	X
	10	0	0	X	X

Thus,

$$T_1 = \overline{Q_3} Q_0.$$

For T_2 :

		Q_1Q_0			
		00	01	11	10
Q_3Q_2	00	0	0	1	0
	01	0	0	1	0
	11	X	X	X	X
	10	0	0	X	X

Thus,

$$T_2 = Q_1 Q_0.$$

For T_3 :

		Q_1Q_0			
		00	01	11	10
Q_3Q_2	00	0	0	0	0
	01	0	0	1	0
	11	X	X	X	X
	10	0	1	X	X

Thus,

$$T_3 = Q_2 Q_1 Q_0 + Q_3 Q_0.$$

Down Counter T Flip-Flops

For T_0 :

Again, $T_0 = 1$ for all cases.

For T_1 :

		Q_1Q_0			
		00	01	11	10
Q_3Q_2	00	0	0	0	1
	01	1	0	0	1
	11	X	X	X	X
	10	1	0	X	X

Thus,

$$T_1 = Q_1 \overline{Q_0} + Q_2 \overline{Q_1} \overline{Q_0} + Q_3 \overline{Q_1} \overline{Q_0}.$$

For T_2 :

		Q_1Q_0			
		00	01	11	10
Q_3Q_2	00	0	0	0	0
	01	1	0	0	0
	11	X	X	X	X
	10	1	0	X	X

Thus,

$$T_2 = Q_2 \overline{Q_1} \overline{Q_0} + Q_3 \overline{Q_1} \overline{Q_0}.$$

For T_3 :

		Q_1Q_0			
		00	01	11	10
Q_3Q_2	00	1	0	0	0
	01	0	0	0	0
	11	X	X	X	X
	10	1	0	X	X

Thus,

$$T_3 = \overline{Q_2} \overline{Q_1} \overline{Q_0}.$$

The Karnaugh maps for Down counter can be simplified further but the reason to leave them as give is, take $T = \overline{Q_1} \overline{Q_0}$ then:

1. $T_0 = 1$
2. $T_1 = Q_1 \overline{Q_0} = T_2$
3. $T_2 = (Q_1 + Q_2)T$
4. $T_3 = \overline{Q_2} T$

Which are easier to make in Circuit

Circuit Diagram

Circuit Diagram for Incrementing

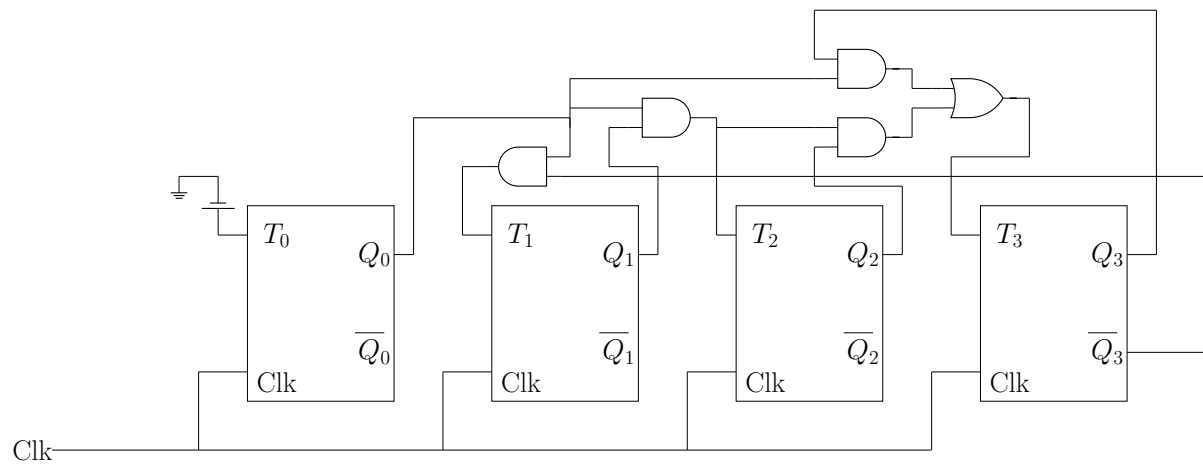


Figure 1: Circuit diagram representing the logic for incrementing.

Let the circuit be represented as:

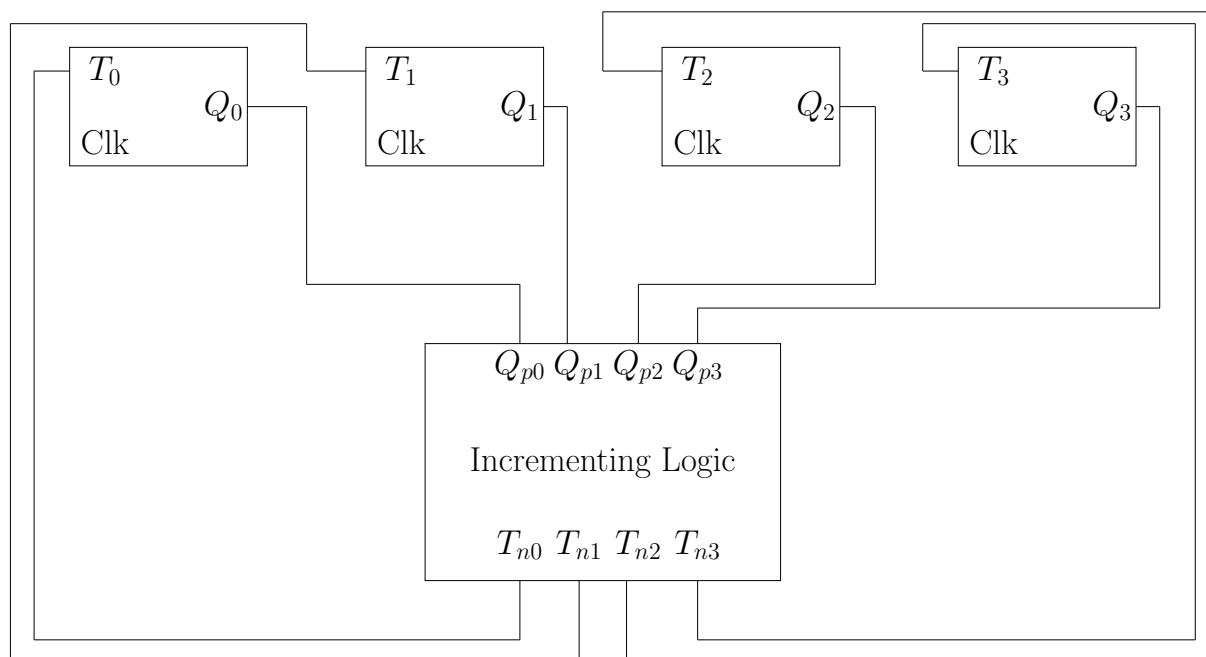


Figure 2: Simplified version of Circuit diagram

Circuit Diagram for Decrementing

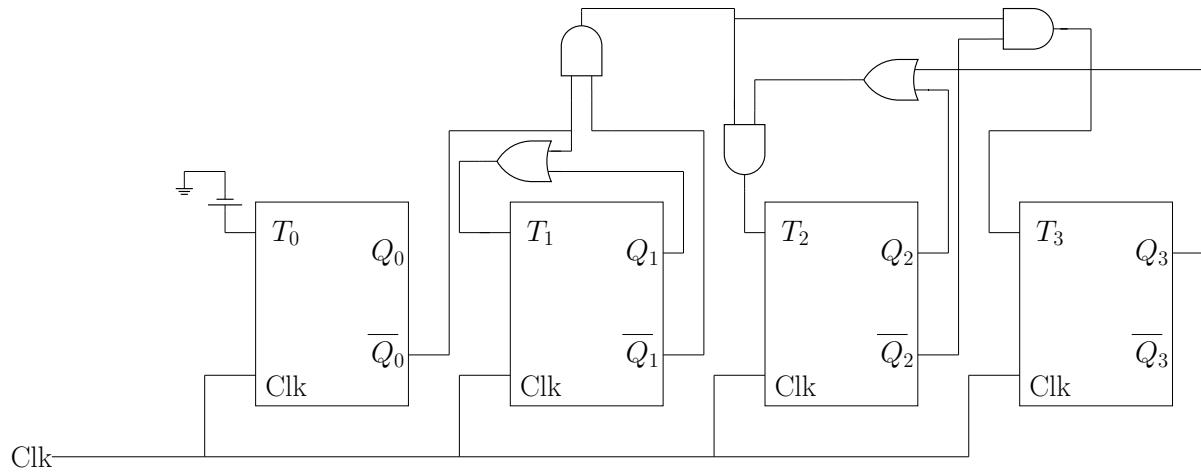


Figure 3: Circuit diagram representing the logic for decrementing.

Let the circuit be represented as:

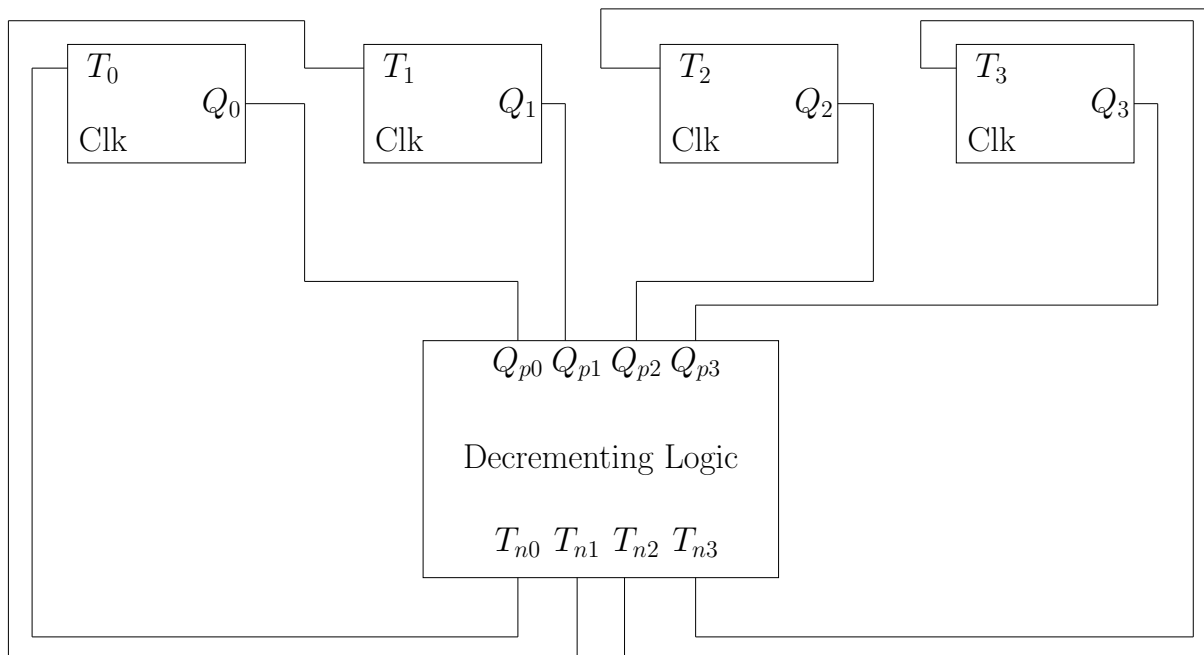


Figure 4: Simplified version of Circuit diagram

Connecting Incrementing and Decrementing Logic

Since we need to activate the Incrementing logic only when the incrementing button B_I is pressed, and activate the Decrementing logic only when the decrementing button B_D is pressed, we pass the Incrementing logic and input of B_I to an AND gate, similarly for Decrementing. Then we will pass outputs of both the AND gates to an OR gate so that whenever B_I is pressed incrementing logic will go through, if B_D is pressed decrementing logic will go through. We will connect clocks of the flip flops to OR of B_I and B_D so that whenever we press a button a pulse will pass activating the flip flops. The Circuit Diagram for this implementation will be:

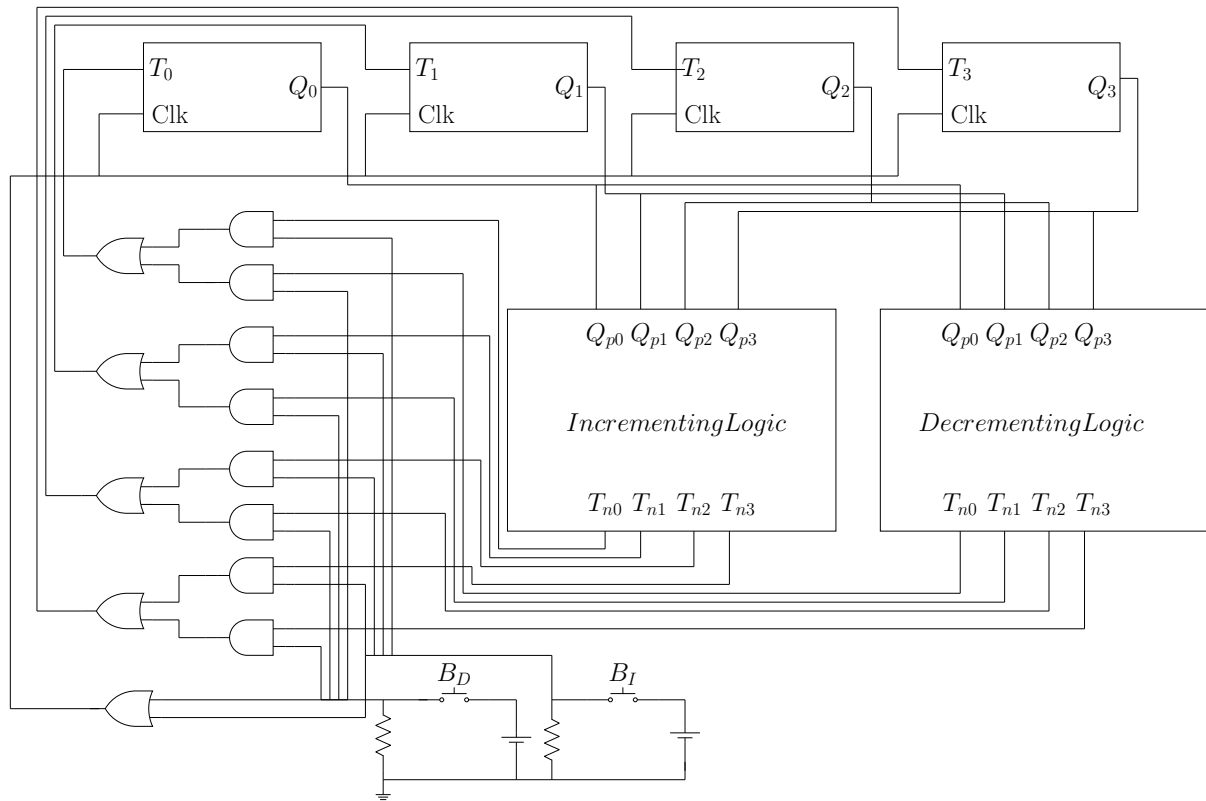


Figure 5: Combining Incrementing and Decrementing for one digit

Let us represent this circuit as:


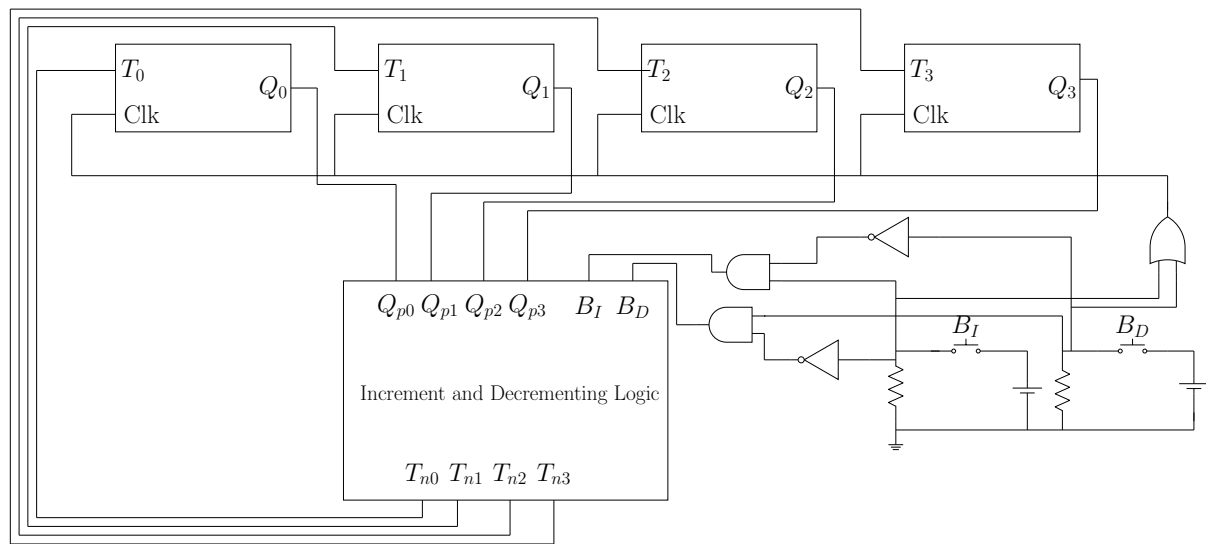


Figure 6: Simplified circuit without Button Logic

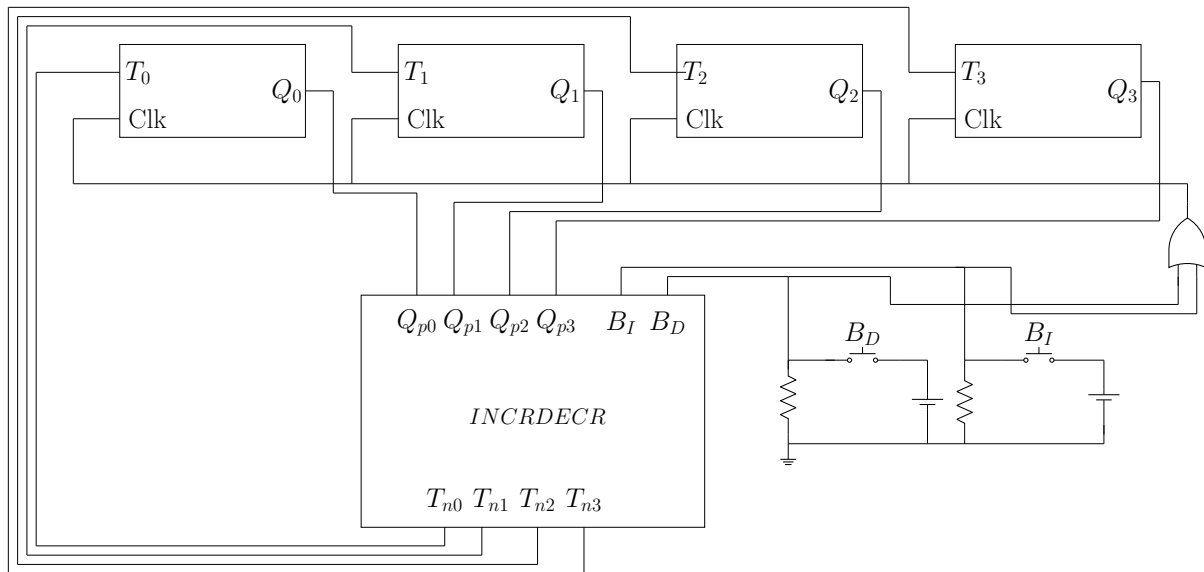The AND and NOT gates which take input as B_I and B_D is a logic so that the circuit increments only when only B_I is pressed, and decrements only when only B_D is pressed. In rest all cases it does nothing. Let us represent the circuit in the following way:



The Entire Circuit

Now that we have the increment and decrement logic for the first digit, For the second digit we will create the exact same circuit but AND the clock with Q_0 , $\overline{Q_1}$, $\overline{Q_2}$, Q_3 of the first digit so that it will only increment when the first digit is 9. The Circuit for that will be as follows:

In the above circuit Q_{ij} represents j^{th} bit of i^{th} digit. That is the BCD number is in the form:

$$Q_{13}Q_{12}Q_{11}Q_{10} \quad Q_{03}Q_{02}Q_{01}Q_{00}$$

Connecting the output to 7447 Decoder and then Connecting the output of that to Seven segment Displays helps us to visualize the output

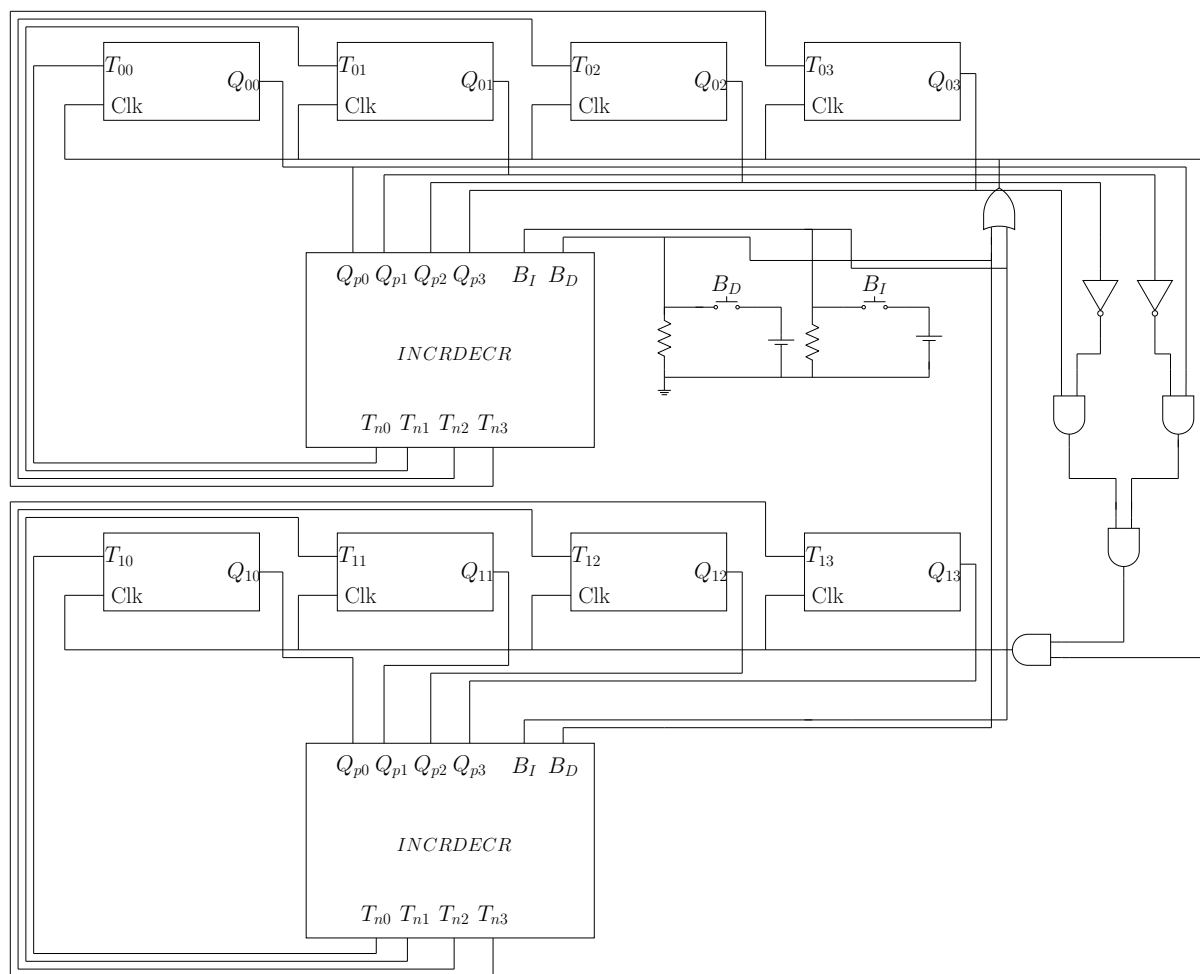


Figure 7: Complete Circuit

Procedure

1. Circuit Setup:

- Connect four T flip-flops (using JK flip-flop ICs configured as T flip-flops) in series to create a 4-bit counter.
- Wire the T inputs according to the derived logic equations.
- Connect one push button to the clock input for up counting and the other through appropriate logic for down counting.
- Connect the outputs (Q_3, Q_2, Q_1, Q_0) to the BCD-to-7-segment decoder.
- Connect the decoder outputs to the 7-segment display.
- Use the oscilloscope and logic analyzer to verify clock signals and state transitions.

2. Testing Up Counter:

- Set the mode control $M = 0$ for up counting.
- Press the up-count button repeatedly and observe the sequence on the 7-segment display.

- Verify that the counter increments from 0 to 9 and then resets to 0.

3. Testing Down Counter:

- Set the mode control $M = 1$ for down counting.
- Press the down-count button repeatedly and observe the sequence.
- Verify that the counter decrements from 9 to 0 and then resets to 9.

4. Verification:

- Test the counter with different starting values.
- Ensure proper transitions between up and down counting modes.

Observations

Up Counter Operation ($M = 0$)

Button Press	$Q_3 Q_2 Q_1 Q_0$	Decimal
Initial	0 0 0 0	0
Press 1	0 0 0 1	1
Press 2	0 0 1 0	2
Press 3	0 0 1 1	3
Press 4	0 1 0 0	4
Press 5	0 1 0 1	5
Press 6	0 1 1 0	6
Press 7	0 1 1 1	7
Press 8	1 0 0 0	8
Press 9	1 0 0 1	9
Press 10	0 0 0 0	0

Down Counter Operation ($M = 1$)

Button Press	$Q_3 Q_2 Q_1 Q_0$	Decimal
Initial	1 0 0 1	9
Press 1	1 0 0 0	8
Press 2	0 1 1 1	7
Press 3	0 1 1 0	6
Press 4	0 1 0 1	5
Press 5	0 1 0 0	4
Press 6	0 0 1 1	3
Press 7	0 0 1 0	2
Press 8	0 0 0 1	1
Press 9	0 0 0 0	0
Press 10	1 0 0 1	9

Conclusion

The BCD counter using T flip-flops was successfully designed and implemented with bidirectional counting capability. The counter correctly counts from 0 to 9 in up mode

and from 9 to 0 in down mode, resetting appropriately at the boundaries. The use of push buttons to select the counting direction, along with a BCD-to-7-segment decoder for display, provides a clear demonstration of sequential logic in digital systems. This design can be extended to applications such as digital clocks, frequency counters, and event counters where bidirectional counting is required.