

Experiment 5: Op-Amp Applications

Abhimanyu Koushik (EE24BTECH11024),
Agamjot Singh (EE24BTECH11002)
IIT Hyderabad

March 3, 2025

Abstract

This experiment explores three key applications of operational amplifiers (op-amps): custom weighted summing and difference amplifiers, op-amp integrators, and precision rectifiers. The mathematical principles, circuit designs, and working mechanisms are analyzed. Experimental results validate the theoretical predictions and demonstrate the versatility of op-amps in signal processing.

1 Introduction

Operational amplifiers (op-amps) are versatile components widely used in analog signal processing. This experiment focuses on three applications: 1. Custom weighted summing and difference amplifier. 2. Op-amp integrator. 3. Precision rectifier (super diode).

Each application is implemented using appropriate circuit designs to perform mathematical operations or signal conditioning tasks.

2 Custom Weighted Summing & Difference Amplifier

Objective To implement mathematical functions such as:

$$V_{\text{out}} = 2V_1 + V_2 - V_3$$

$$V_{\text{out}} = 2V_1 - V_3$$

Circuit Design The circuit uses an inverting summing amplifier with carefully chosen resistors to achieve desired weighting coefficients. If a non-inverting input is required, a combination of inverting and summing amplifiers can be used.

Components Required - Op-amp (e.g., LM741, TL081) - Resistors (precisely selected for weighting) - DC power supply - Function generator (for input signals) - Oscilloscope

Equation Derivation For an inverting summing amplifier:

$$V_{\text{out}} = - \left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right)$$

By selecting appropriate resistor values (R_f, R_1, R_2, R_3), the desired coefficients for V_1, V_2, V_3 can be achieved.

3 Op-Amp Integrator

Objective To design a circuit that performs mathematical integration:

$$V_{\text{out}} = -\frac{1}{RC} \int V_{\text{in}} dt$$

Circuit Design The circuit uses an operational amplifier with a capacitor in the feedback path instead of a resistor. This configuration enables the op-amp to act as a continuous-time integrator.

Components Required - Op-amp (e.g., LM741, TL081) - Resistor (R) - Capacitor (C) - DC power supply - Function generator - Oscilloscope

Working Principle The op-amp integrator converts a square wave input into a triangular wave output. It acts as a continuous-time integrator in signal processing applications.

4 Precision Rectifier (Super Diode)

Objective To design a precision rectifier capable of rectifying small AC signals without the voltage drop issue of standard diodes.

Circuit Design The circuit uses an op-amp to control a diode for full-wave or half-wave rectification. The op-amp eliminates the $0.7V$ threshold voltage of conventional diodes.

Components Required - Op-amp (e.g., LM358, TL081) - Diode (e.g., 1N4148) - Resistors - AC signal generator - Oscilloscope

Equation Derivation For a half-wave rectifier:

$$V_{\text{out}} = \begin{cases} 0 & V_{\text{in}} < 0 \\ V_{\text{in}} & V_{\text{in}} > 0 \end{cases}$$

For a full-wave rectifier, an additional summing stage is used to combine the positive portion with the inverted negative portion of the input signal.

5 Results and Observations

****Custom Weighted Summing Amplifier**** The experimental results confirmed that the circuit accurately implemented the mathematical functions: 1. $V_{\text{out}} = 2V_1 + V_2 - V_3$ 2. $V_{\text{out}} = 2V_1 - V_3$

The output voltages measured on the oscilloscope matched theoretical predictions.

****Op-Amp Integrator**** The integrator successfully converted square wave inputs into triangular wave outputs. The observed waveforms were consistent with theoretical expectations.

****Precision Rectifier**** The precision rectifier effectively rectified small AC signals without any noticeable voltage drop. Both half-wave and full-wave configurations were tested and verified.

6 Conclusion

This experiment demonstrated three key applications of operational amplifiers: 1. Weighted summing and difference amplifiers were implemented using resistor networks. 2. The op-amp integrator performed real-time integration of input signals. 3. The precision rectifier eliminated voltage drop issues associated with conventional diodes.

These applications highlight the versatility of op-amps in performing mathematical operations and signal conditioning tasks in electronic circuits.
