

Bandpass Filter using Sallen-Key Second-Order Filters

Abhimanyu Koushik (EE24BTECH11024),
Agamjot Singh (EE24BTECH11002)
IIT Hyderabad

March 19, 2025

1 Introduction

Bandpass filters are essential components in signal processing systems, allowing frequencies within a specific range to pass while attenuating frequencies outside this range. This experiment focuses on implementing a bandpass filter using the Sallen-Key topology, which is widely used for its simplicity and stability. The bandpass filter is constructed by cascading a high-pass filter (HPF) and a low-pass filter (LPF), with carefully selected cutoff frequencies to define the desired passband.


2 Theory

2.1 Bandpass Filter Fundamentals

A bandpass filter (BPF) allows signals within a specific frequency range to pass while attenuating signals outside this range. The filter is characterized by:

- Lower cutoff frequency (f_l): Frequencies below this are attenuated
- Upper cutoff frequency (f_h): Frequencies above this are attenuated
- Bandwidth = $f_h - f_l$
- Center frequency (f_0) = $\sqrt{f_h \times f_l}$

2.2 High Pass Filter Topology

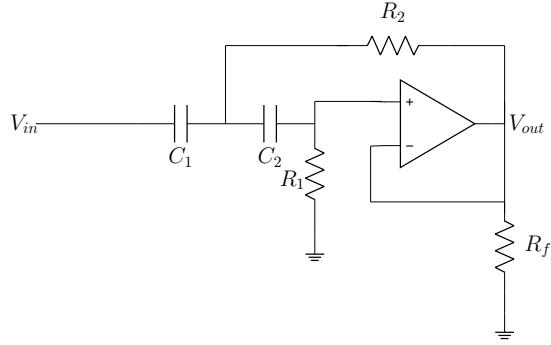

Given the circuit diagram, we write the equations as follows:

$$\frac{V_{in} - V_1}{X_{C_1}} + \frac{V_2 - V_1}{X_{C_2}} + \frac{V_{out} - V_1}{R_2} = 0$$

Simplifying:

$$\frac{V_{in}}{X_{C_1}} + \frac{V_2}{X_{C_2}} + \frac{V_{out}}{R_2} = V_1 \left(\frac{1}{X_{C_1}} + \frac{1}{X_{C_2}} + \frac{1}{R_2} \right)$$

Next, consider the relationship between V_1 and V_2 :

$$\frac{V_1 - V_2}{X_{C_2}} - \frac{V_2}{R_1} = 0$$

Rewriting:

$$V_1 = V_2 \left(1 + \frac{X_{C_2}}{R_1} \right)$$

Using the virtual short property ($V_2 = V_{out}$):

$$V_1 = V_{out} \left(1 + \frac{X_{C_2}}{R_1} \right)$$

Substituting X_{C_1} and X_{C_2} as:

$$X_{C_1} = \frac{1}{j\omega C_1}, \quad X_{C_2} = \frac{1}{j\omega C_2}$$

We get:

$$V_1 = V_{\text{out}} \left(1 + \frac{1}{j\omega C_1 R_2} \right)$$

Substituting back into the first equation:

$$\frac{V_{\text{in}}}{X_{C_1}} + \frac{V_{\text{out}}}{R_2} + j\omega C_2 V_{\text{out}} = V_{\text{out}} \left(1 + \frac{1}{j\omega C_1 R_2} \right) \left(\frac{1}{R_2} + j\omega C_1 + j\omega C_2 \right)$$

Expanding further:

$$\frac{V_{\text{in}}}{X_{C_1}} + V_{\text{out}} \left(\frac{1}{R_2} + j\omega C_2 \right) = V_{\text{out}} \left(1 + \frac{1}{j\omega C_1 R_2} \right) \left(\frac{1}{R_2} + j\omega C_1 + j\omega C_2 \right)$$

Rewriting the transfer function:

$$s^2 V_{\text{in}} C_1 C_2 R_1 R_2 = V_{\text{out}} \left(1 + sR_2(C_1 + C_2) + s^2 C_1 C_2 R_1 R_2 \right)$$

$$H(s) = \frac{V_{\text{out}}}{V_{\text{in}}} = \frac{s^2 C_1 C_2 R_1 R_2}{s^2 C_1 C_2 R_1 R_2 + sR_2(C_1 + C_2) + 1}$$

Assume $C_1 = C_2 = C$ and $R_1 = R_2 = R$,

$$\text{Gain} = |H(s)| = \frac{(\omega RC)^2}{(\omega RC)^2 + 1}$$


Cutoff angular frequency (ω_c) is given by,

$$\omega_c = \frac{1}{RC}$$

Cutoff frequency (f_c) is given by,

$$f_c = \frac{1}{2\pi RC}$$

2.3 Low-Pass Filter Topology

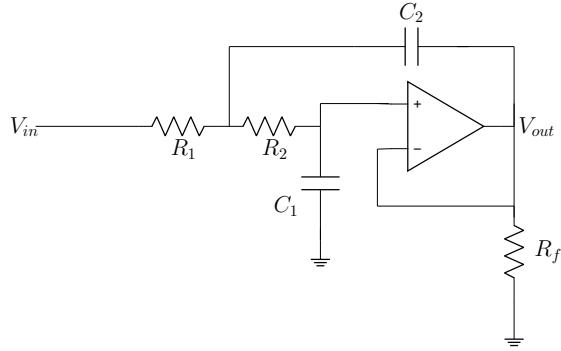

Given the circuit diagram, we write the equations as follows:

$$\frac{V_{in} - V_1}{R_1} + \frac{V_2 - V_1}{R_2} + \frac{V_{out} - V_1}{X_{C_2}} = 0 \quad (1)$$

Simplifying:

$$\frac{V_{in}}{R_1} + \frac{V_2}{R_2} + \frac{V_{out}}{X_{C_2}} = V_1 \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{X_{C_2}} \right) \quad (2)$$

Next, consider the relationship between V_1 and V_2 :

$$\frac{V_1 - V_2}{R_2} - \frac{V_2}{X_{C_1}} = 0 \quad (3)$$

Rewriting:

$$V_1 = V_2 \left(1 + \frac{R_2}{X_{C_1}} \right) \quad (4)$$

Using the virtual short property ($V_2 = V_{out}$):

$$V_1 = V_{out} \left(1 + \frac{R_2}{X_{C_1}} \right) \quad (5)$$

Substituting X_{C_1} and X_{C_2} as:

$$X_{C_1} = \frac{1}{j\omega C_1}, \quad X_{C_2} = \frac{1}{j\omega C_2} \quad (6)$$

We get:

$$V_1 = V_{\text{out}} (1 + j\omega C_1 R_2) \quad (7)$$

Substituting back into the first equation:

$$\frac{V_{\text{in}}}{R_1} + \frac{V_{\text{out}}}{R_2} + j\omega C_2 V_{\text{out}} = V_{\text{out}} (1 + j\omega C_1 R_2) \left(\frac{1}{R_1} + \frac{1}{R_2} + j\omega C_2 \right) \quad (8)$$

Expanding further:

$$\frac{V_{\text{in}}}{R_1} + V_{\text{out}} \left(\frac{1}{R_2} + j\omega C_2 \right) = V_{\text{out}} (1 + j\omega C_1 R_2) \left(\frac{1}{R_1} + \frac{1}{R_2} + j\omega C_2 \right) \quad (9)$$

Rewriting the transfer function:

$$V_{\text{in}} = V_{\text{out}} (1 + sC_1(R_1 + R_2) + s^2 C_1 C_2 R_1 R_2) \quad (10)$$

$$H(s) = \frac{V_{\text{out}}}{V_{\text{in}}} = \frac{1}{s^2 C_1 C_2 R_1 R_2 + s C_1 (R_1 + R_2) + 1} \quad (11)$$

Assume $C_1 = C_2 = C$ and $R_1 = R_2 = R$,

$$\text{Gain} = |H(s)| = \frac{1}{(\omega RC)^2 + 1}$$

Cutoff angular frequency (ω_c) is given by,


$$\omega_c = \frac{1}{RC}$$

Cutoff frequency (f_c) is given by,

$$f_c = \frac{1}{2\pi RC}$$

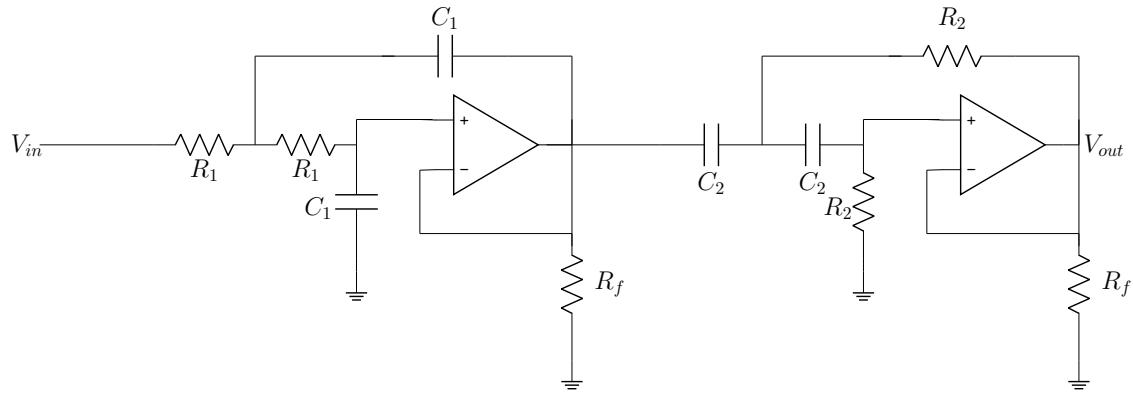2.4 Band-Pass Filter Topology

Band-Pass Filter is just low-pass and high-pass filters cascaded, i.e. output of low-pass filter is passed to high-pass filter and the final out is V_{out} of high-pass filter.



Cutoff frequency (low-pass): $f_{low} = \frac{1}{R_1 C_1}$.

Cutoff frequency (high-pass): $f_{high} = \frac{1}{R_2 C_2}$.

Bandwidth = $f_{low} - f_{high} = \frac{1}{R_1 C_1} - \frac{1}{R_2 C_2}$.

3 Apparatus

- Operational Amplifiers
- Resistors: R_1, R_2, R_3, R_4 (in $k\Omega$)
- Capacitors: C_1, C_2, C_3, C_4 (in nF)
- Function Generator
- Oscilloscope
- DC Power Supply
- Breadboard and connecting wires

4 Procedure

4.0.1 High-Pass Filter Implementation

1. Assemble the Sallen-Key HPF circuit on the breadboard.

2. Connect the function generator to the input and set it to generate a sine wave.
3. Connect the oscilloscope to measure the output voltage.
4. Vary the input frequency from 100 Hz to 100 kHz in appropriate steps.
5. For each frequency, record the input and output voltages to calculate the gain.
6. Plot the frequency response (gain vs. frequency) on a logarithmic scale.

4.0.2 Low-Pass Filter Implementation

1. Assemble the Sallen-Key LPF circuit on the breadboard.
2. Repeat the same procedure as in Step 1.

4.0.3 Bandpass Filter Implementation

1. Connect the output of the LPF to the input of the HPF to form the complete bandpass filter.
2. Repeat the frequency response measurements as in the previous steps.


5 Results and Analysis

5.1 Low-Pass Filter


$$R = 1k\Omega, C = 85nF$$

$\log(\omega)$	$20 \log(H(s))$
1.7982	-0.7242
2.4971	0.0
2.7982	0.0
3.0992	0.0
3.4971	-0.3546
3.7013	-1.1103
3.7982	-1.9382
3.8774	-2.2905
3.9743	-3.6593
4.0992	-5.8112
4.2753	-10.5683
4.4002	-14.3340
4.4971	-16.8328
4.5763	-19.0156
4.6732	-21.9382
4.7982	-25.0362



Table 1: Logarithmic frequency response data for low-pass filter

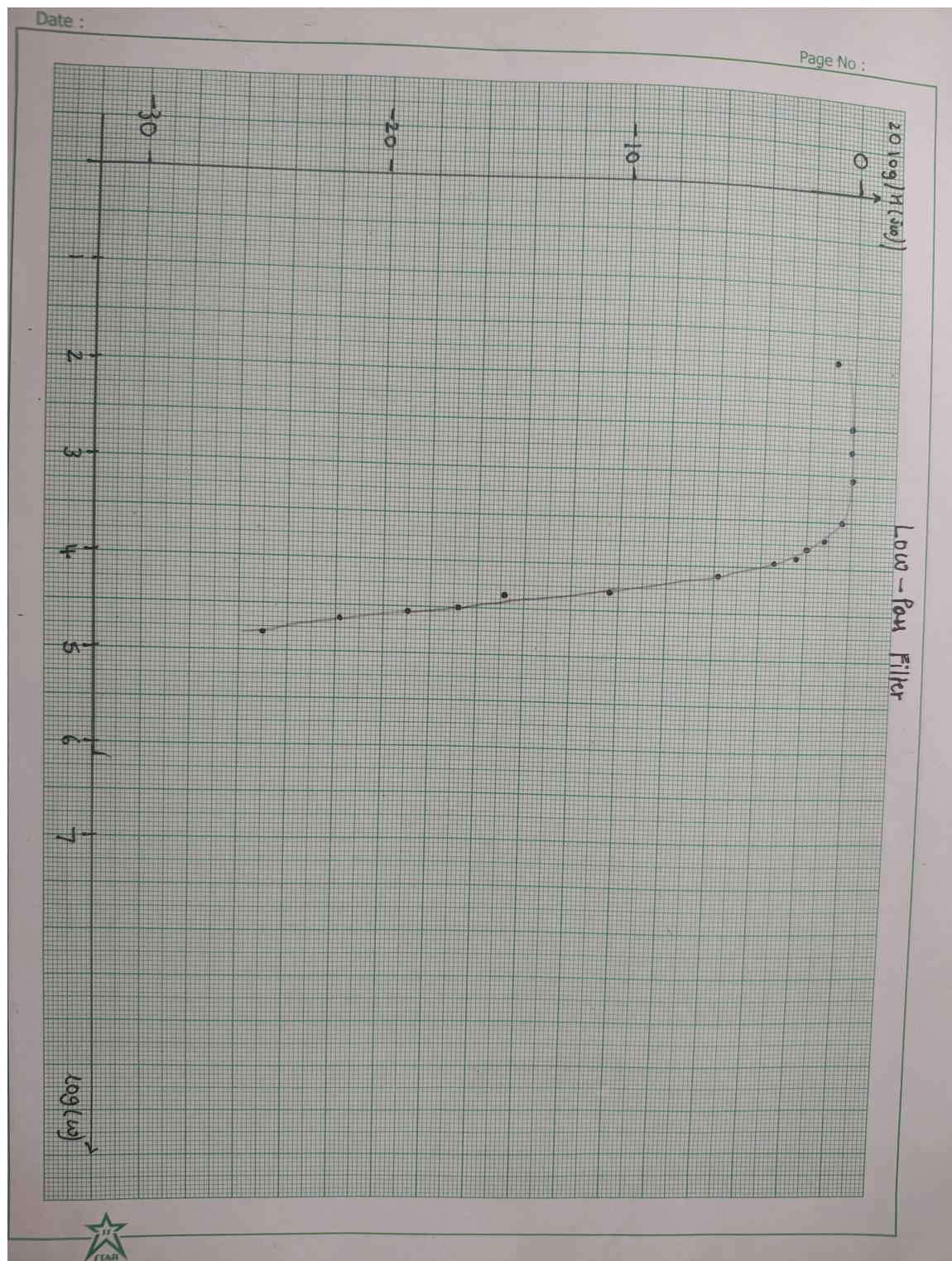

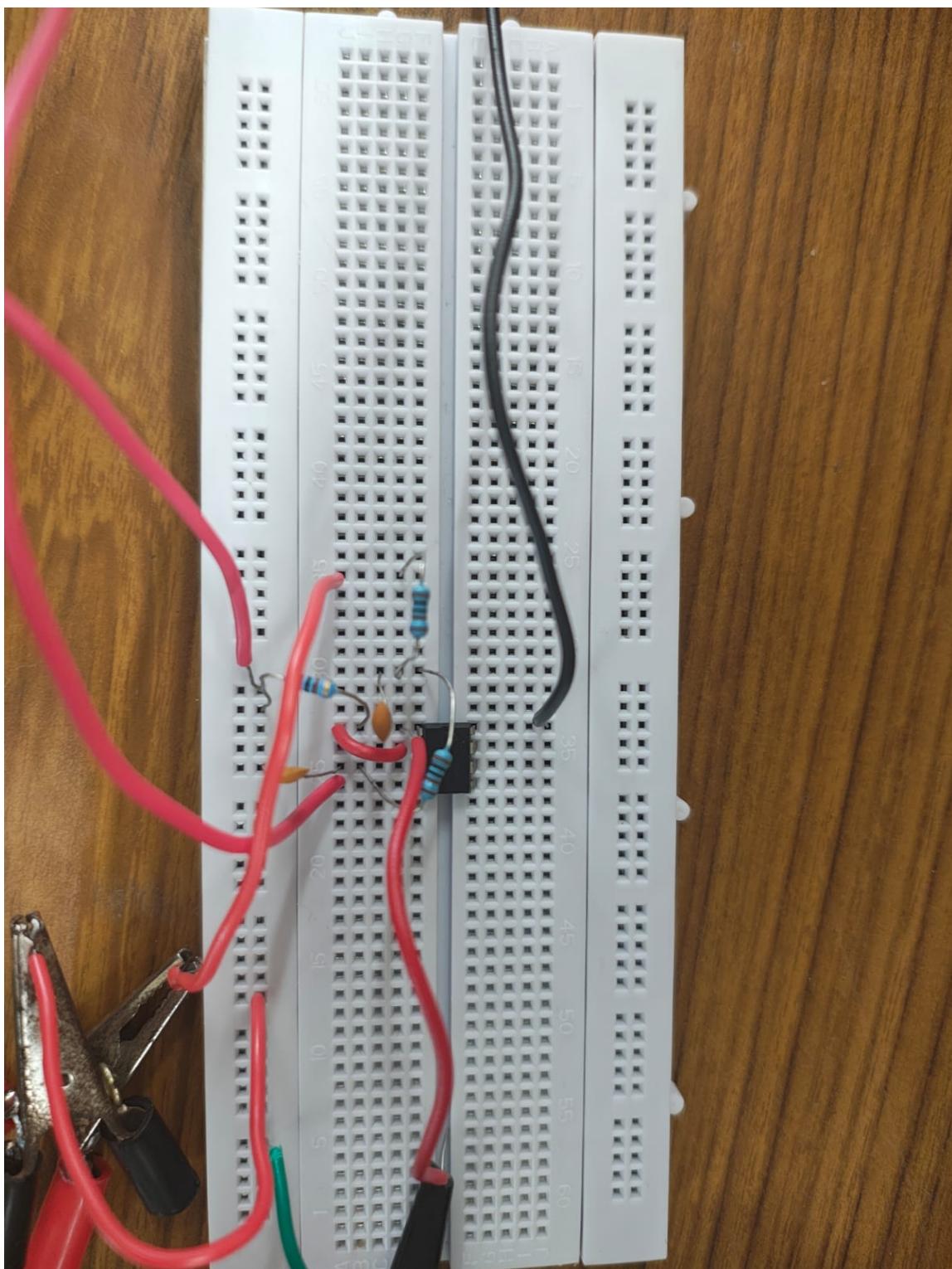9
Figure 1: Bode Plot for Low-Pass Filter



10
Figure 2: Circuit for Low-Pass Filter

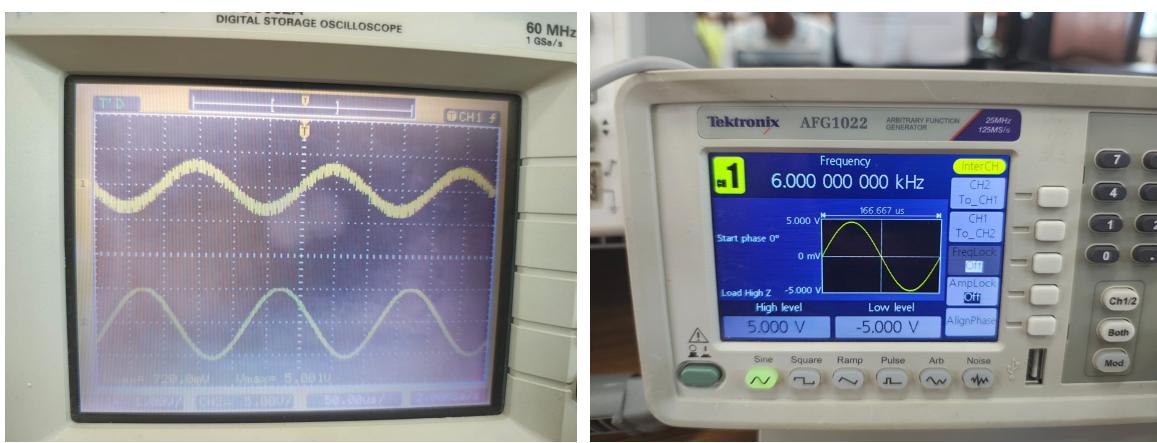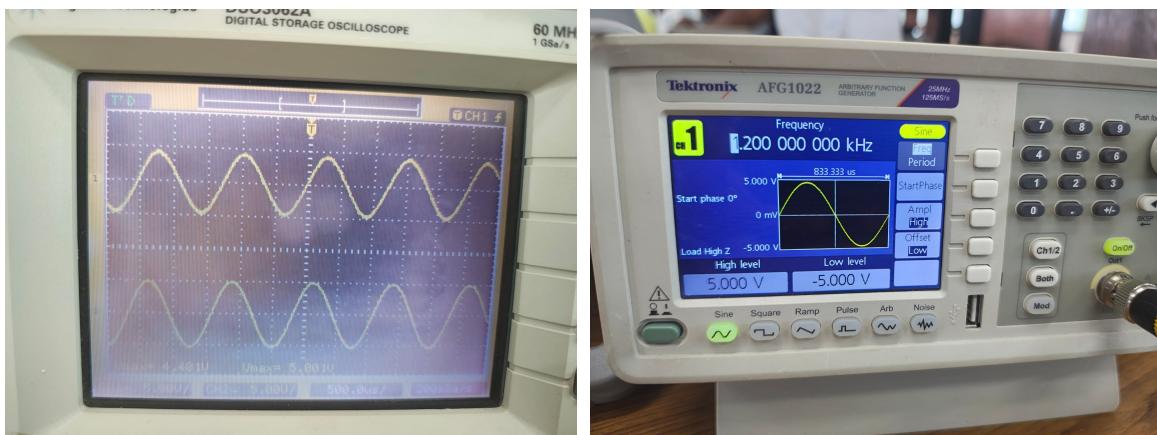


5.2 High-Pass Filter

$$R = 1k\Omega, C = 220nF$$

$\log(\omega)$	$20 \log(H(s))$
3.0992	-20.3546
3.2753	-15.4938
3.4971	-9.4680
3.5763	-7.2863
3.6433	-6.0869
3.7982	-3.6593
4.0992	-1.9360
4.4971	-1.1084
4.7982	-1.1084

Table 2: Logarithmic frequency response data for high-pass filter

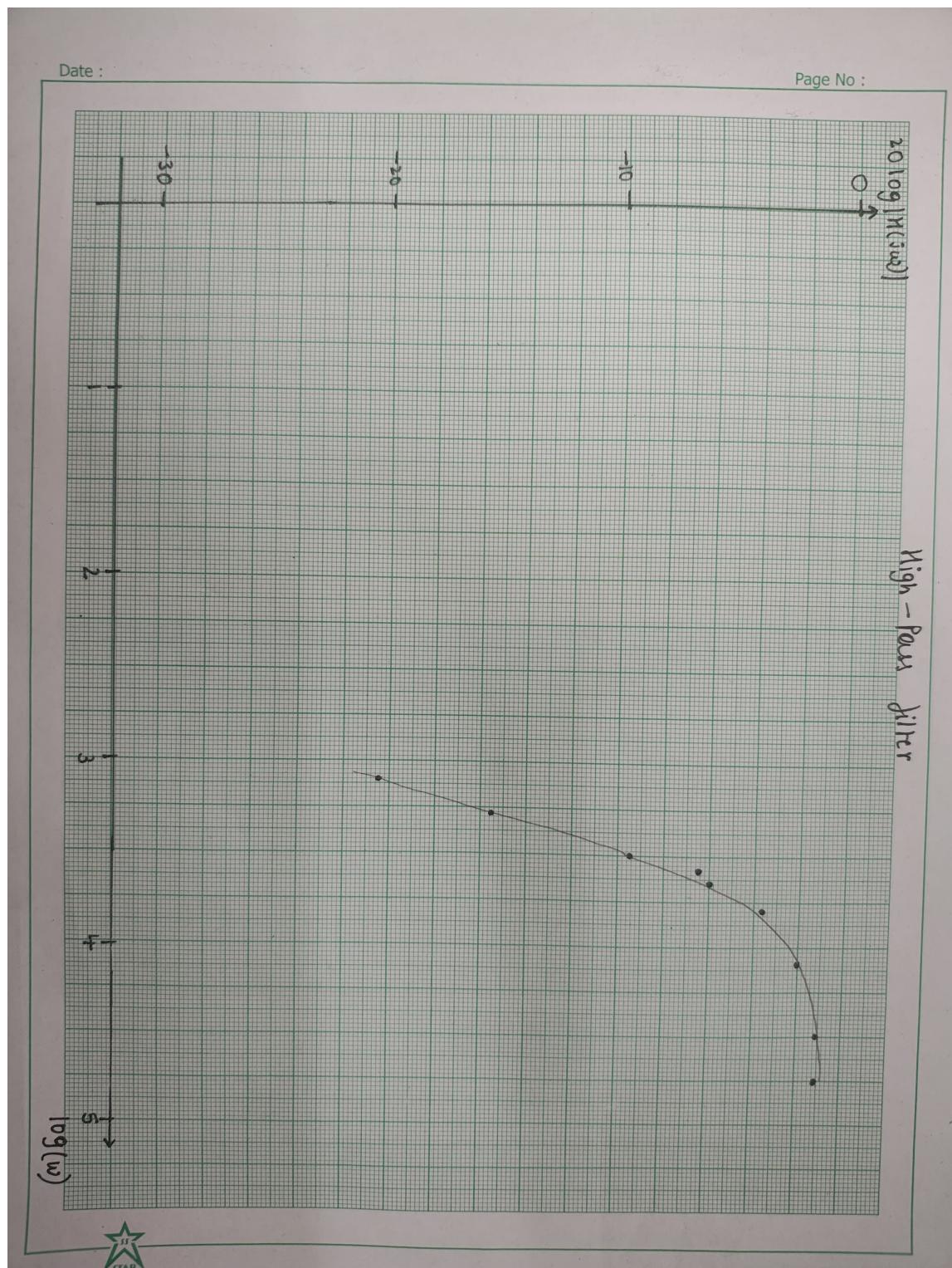

13
Figure 3: Bode Plot for High-Pass Filter


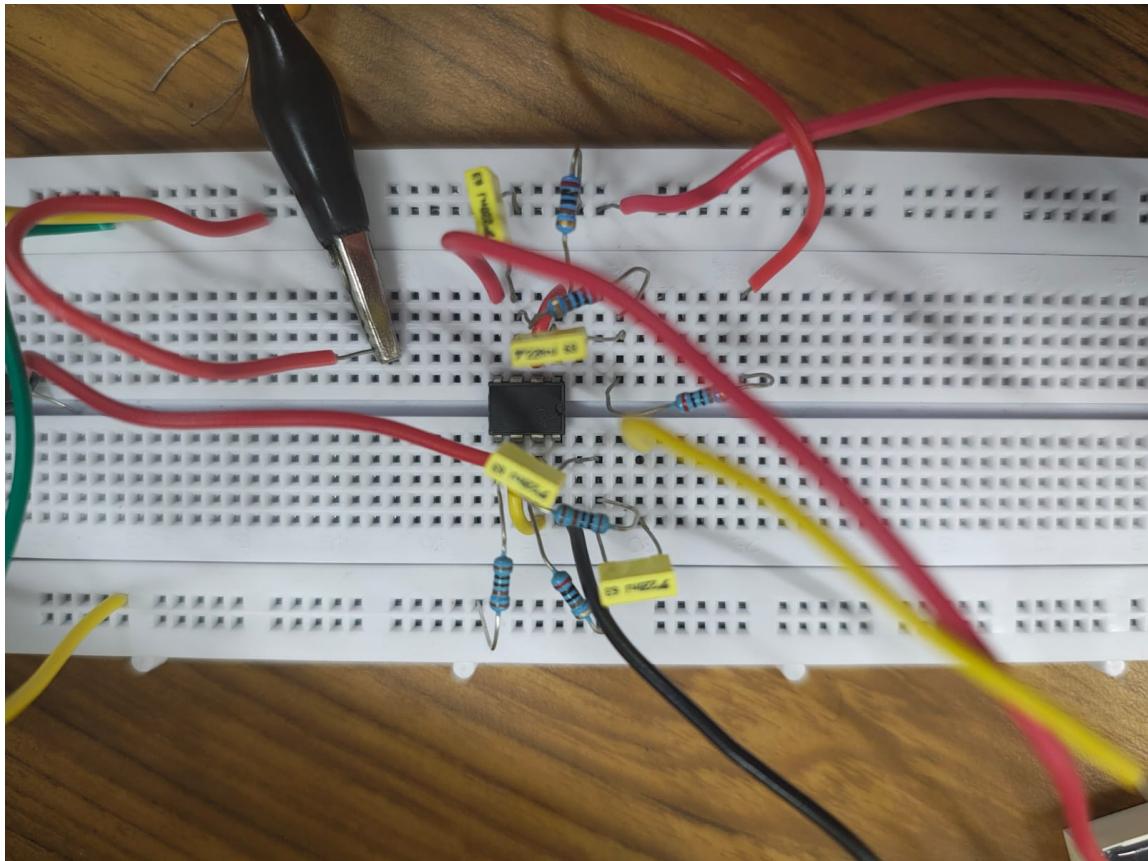


Figure 4: Circuit for High-Pass Filter

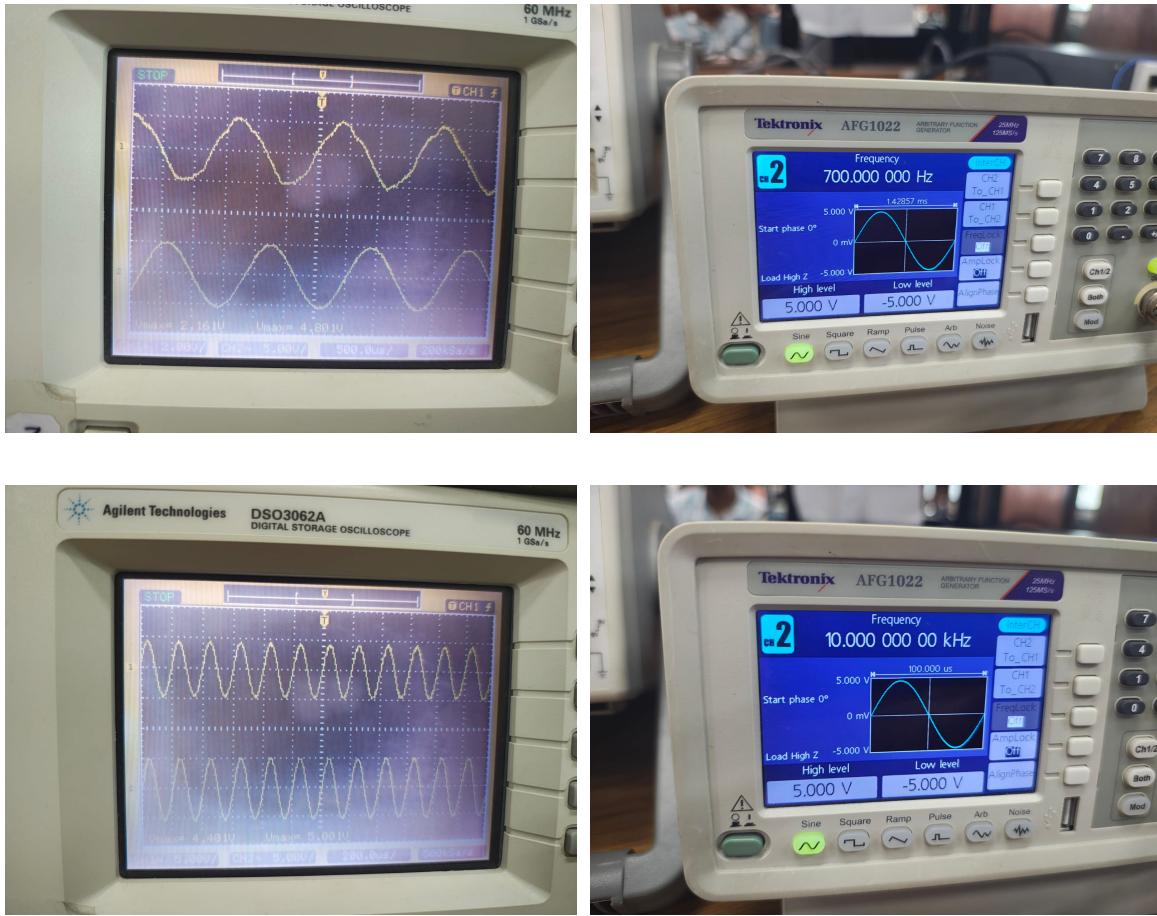



5.3 Band-Pass Filter


Let R_1, C_1 be for Low-Pass filter, and R_2, C_2 be for High-pass Filter.

$$R_1 = 1k\Omega, C_1 = 200nF$$

$$R_2 = 4.7k\Omega, C_2 = 200nF$$

$\log(\omega)$	$20 \log(H(s))$
2.4971	-16.8328
2.6433	-13.6309
2.7982	-9.6772
2.9743	-5.8112
3.0992	-4.0935
3.1961	-3.0461
3.4002	-2.6601
3.4971	-3.2457
3.5763	-4.0963
3.7982	-7.9545
3.9743	-11.8281
4.0992	-15.9176
4.2753	-19.6593
4.4971	-23.2482

Table 3: Logarithmic frequency response data for band-pass filter

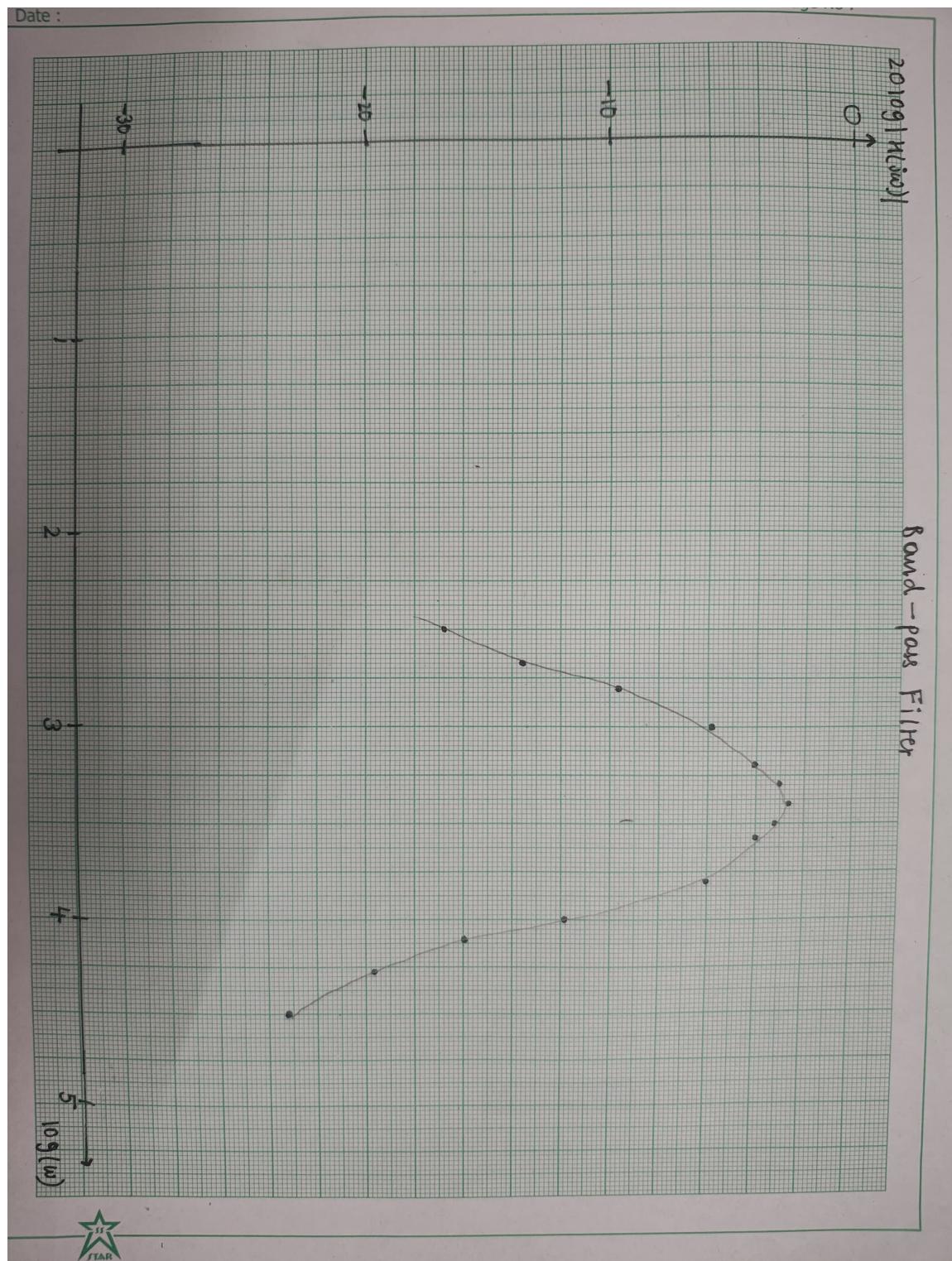

17
Figure 5: Bode Plot for Band-Pass Filter


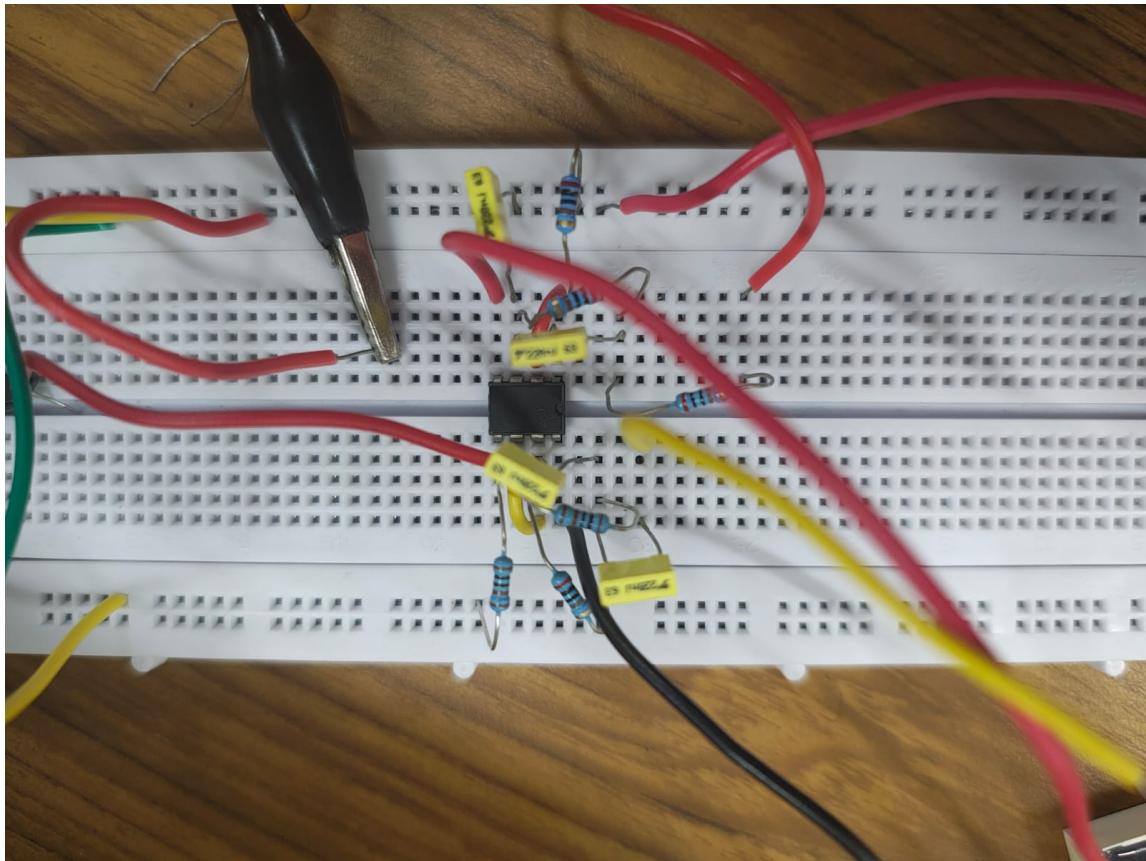


Figure 6: Circuit for Band-Pass Filter

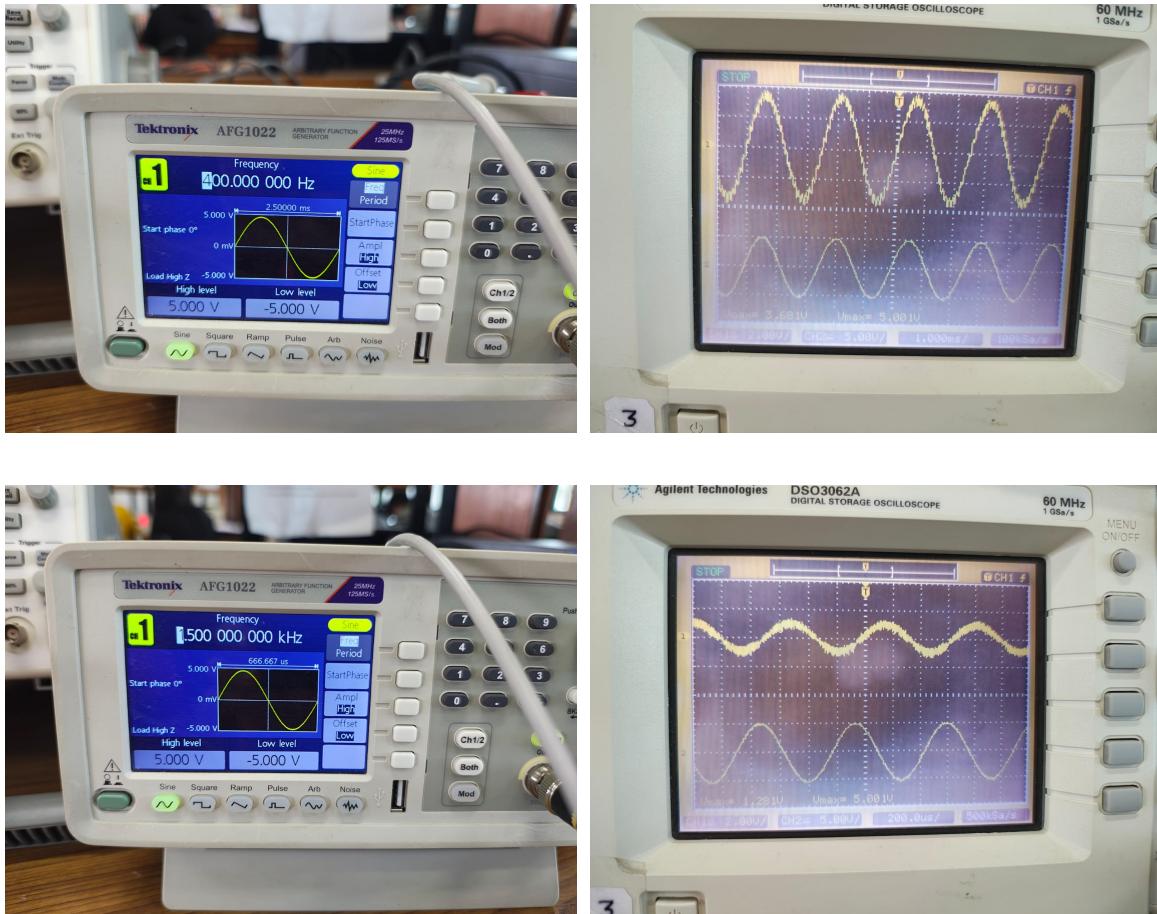



6 Verification Codes and Pictures

All the pictures taken are provided below, <https://github.com/AbhimanyuKoushik/EE1200/tree/main/Lab6/Pictures>

Python verification codes are provided below, <https://github.com/AbhimanyuKoushik/EE1200/tree/main/Lab6>

7 Conclusion

This experiment successfully demonstrated the design and implementation of a band-pass filter using cascaded Sallen-Key second-order filters.

The Sallen-Key topology proved to be an effective and practical solution for implementing active filters with predictable characteristics. The cascading method for creating a bandpass filter from high-pass and low-pass sections was verified to be a viable approach.